

Electronics Projects Circuits

Search!

Search ...



Categories

- [Mini Projects](#) (247)
- [Inverters](#) (22)
- [Battery & Charger](#) (27)
- [Power supply](#) (136)
- [DC converters](#) (39)
- [Basic Circuits](#) (201)
- [Amplifiers](#) (151)
- [Controls & Timers](#) (122)
- [Lightings](#) (90)
- [Meters & Detectors](#) (108)
- [Digitals](#) (86)
- [RF – Oscillator](#) (81)
- [DIY Electronics](#) (40)
- [Alarm systems](#) (61)
- [Audio diagram](#) (80)
- [Automotive](#) (17)
- [Basic – Tools & Tips](#) (80)
- [Hobby Electronic Projects](#) (45)

Recent Posts



Simple Electronic Stethoscope circuits

August 26, 2017 1



Simple time Delay Circuit using MOSFET

August 23, 2017 8



Mini emergency light circuits

August 16, 2017 0



Electronic siren circuits using transistors

August 14, 2017 7

[Home](#) ▶ [Mini Projects](#) ▶ Digital multimeter circuit using ICL7107

Digital multimeter circuit using ICL7107

Mini Projects Meters & Detectors Admin February 15, 2015 14

[Electronic Test equipments, ICL7107](#)

This is Digital multimeter circuit using ICL7107. We can modify the dc digital meter circuit to smart full function multimeter, that versatile available. For example : measure DC voltage, AC DC Amp meter, AC Amp meter and as the Ohms meter etc.

Try to build this projects to use it really worth Fully enjoy

Special Feature

DC Voltage: 200mV, 2V, 20V, 200V, 2KV, 20KV

AC Voltage: 200mV, 2V, 20V, 200V, 2KV, 20KV

DC Amp: 200uA, 2mA, 20mA, 2A, 10A

AC Amp: 200uA, 2mA, 20mA, 2A, 10A

Ohms meter: 200, 2K, 20K, 200K, 2M, 20M

DC voltage measurement

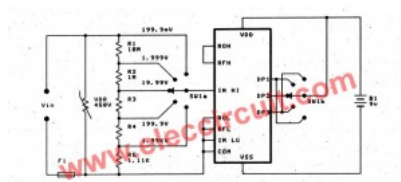


Figure 1 DC voltage measurement

In Figure 1 the schematic diagram of this project. Of course, the easiest way is used as the voltage meter circuit.

The characteristics of the circuit That can measure voltages up to 200mV. We can be apply measure the voltage range higher. As circuit is shown in table 1

R1	R2	R3	R4	R5	INPUT Z.
9M	100K	10K	10K	1K	10M
10M	1M	100K	10K	1.1K	11.1M

Table 1 is shown in the resistance at various ranges.

Note: We may choose resistors in both formats. For the very high voltage measurement. It is necessary to use the external high voltage probe.

Note: R3=100K ; R4=10K

DC current measurement

Next take a look at the simple DC Ammeter circuit is Design appropriate determine the resistance in parallel with the input of the digital meter only.

The principle to calculate the resistance is The voltage caused by the flow of current across resistor in each range is maximum up to 200mV as show in Figure 2

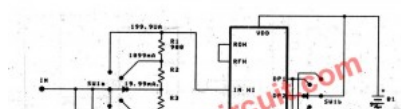


Figure 2 DC Ammeter circuit

In Figure 2 is a circuit that is designed to have a range of up to 5 range. For the high current measurement 2 Amperes, Should the input separately, because the contact of switch that cannot withstand currents.

Diode D1, D2, overload protection is provided for the input.

Note: $R_2 = 90\ \Omega$, $R_3 = 9\ \Omega$

AC voltage measurement

We can design the AC voltage measurement circuit. By add the AC to DC converter circuit that has the together relationship as show in Figure 3.

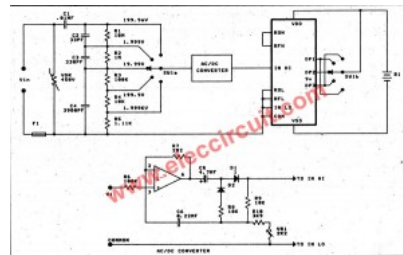


Figure 3 the AC voltmeter circuit

The AC voltage is measured to reduce voltage same the DC voltmeter circuit. Then fed to the AC to DC converter circuit by IC1 and accessories in Figure 3.

VR1 serves as a tune to the correct voltage reading.

AC current measurement

The same principle applies to the DC voltmeter circuit. We can be applied to the AC ammeter adding the AC to DC converter before as show in Figure 4

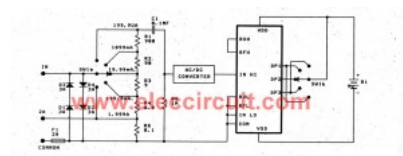


Figure 4 AC current measurement

Ohms meter

advantaged that our digital meter better the regular meter. The reading was accurate, and can also be used to measure the resistance of 0.1 ohms or less, such as high as 10M easily, by the circuit connection as shown in Figure 5.


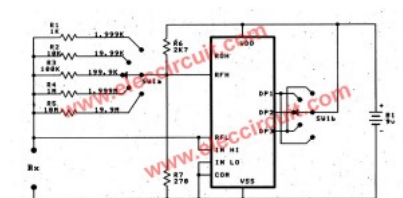


Figure 5 the ohms meter circuit

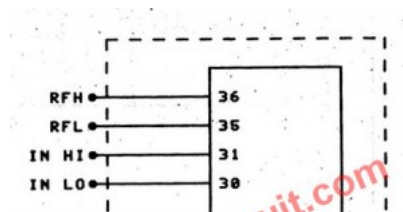

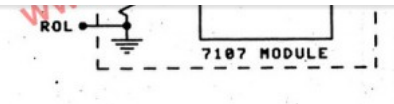


Figure 6 the ICL7107 module

The digital meter module in Figure 1-5 We have shown for the legs of the circuit ICL7107. Compared to the legs of the modules to Easy to write all the circuits. The ROH pin is the out reference voltage at middle leg of the horseshoe-shaped resistor

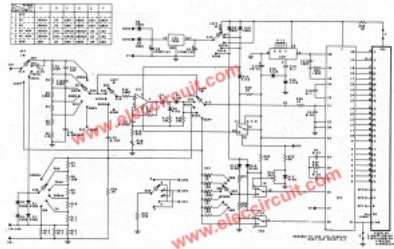


Figure 7 the full circuit diagram of digital multimeter

In Figure 7 is a circuit work perfectly by show PCB layout and the components as show in Figure 8, which can be used to create a user-friendly way.

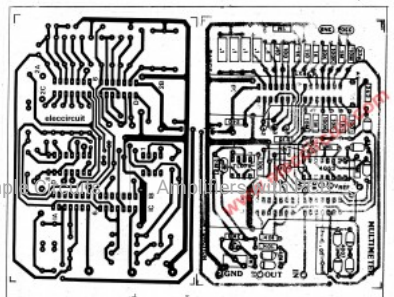


Figure 8 the pcb layout and components layout

Parts you will needs.

IC1___TL071___Operational Amplifiers – Op Amps JFET Input Low Noise

IC5___LM7805___Standard Regulator 5 Volt 1 Amp 3 Pin 3+ Tab TO-220

IC3___CD4049___CMOS Hex Inverting Buffer/Converter

IC2___CD4066___Quad Analog Switch/Multiplexer/Demultiplexer

IC4___ICL7107 or ICL7106___Analog to Digital Converter Single Dual Slope 0.003k SPS 3 1

Digit LED 40-Pin PDIP

LED 7 segment or LCD display

More Switches please read in text

Resistors tolerance: 1%

R1,R26_____10M 0.5 watts

R2,R25,R30,R33,R36,R38___1M 0.5 watts

R3,R15,R24_____100K 0.5 watts

R4,R19,R20,R23_____10K 0.5 watts

R5,R22_____1K 0.5 watts

R6_____110 ohms

R7_____1K 0.5 Watts

R8_____100 ohms 0.5 watts

R9_____10 ohms 0.5 watts

R10_____1 ohms 1 watts

R11,R12,R13,R14_____0.1 ohms 2 watts

R16_____3.3K 0.5 watts

R17,R27_____2.2K 0.5 watts

R21_____100 ohms 0.5 watts

R28_____270 ohms 0.5 watts

MKT capacitors

C14_____33pF 63V

C15_____330pF 63V

C16_____0.0039uF 63V

C11_____100pF 63V

C10_____0.1uF 63V

C9_____0.01uF 63V

C8_____0.47uF 63V

C7_____0.22uF 63V

Electrolytic capacitors

C5,C6_____470uF 16V

C13_____10uF 16V

Diodes

D1-D4_____1N5408

D7,D8,D9,D10_____1N4001

D5,D6,D11,D12,D13,D14,D15_____1N4148

Switch see in circuit and PCB layout











Share 0 Tweet     Email

JLCPCB Prototype: \$2 for 10 pcs PCBs (2-layer,100x100mm)

China's Largest PCB Manufacturer, 290,000+ Customers & 8,000+ Online Orders Per Day

PCB Instant Quote: <https://jlcpcb.com/quote>

Related Posts

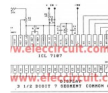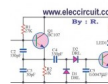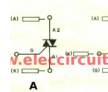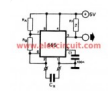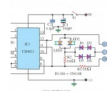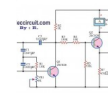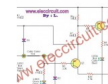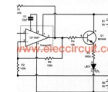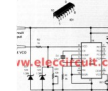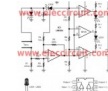[Digital voltmeter using ICL7107](#)[Crystal tester circuit using BC107](#)[Simple SCR tester circuit diagram](#)[Simple capacitance measurement circuit using IC-555](#)[Simple transistor tester circuits](#)[Flyback transformer tester circuit using 2SC828](#)[Coaxial cable tester circuit](#)[The Op-amp IC tester circuit](#)[Universal tester circuit with VCO\(voltage controlled oscillator\)](#)[The food salt & salinity tester meter circuit](#)[◀ PREVIOUS POST](#)[NEXT POST ▶](#)

14 COMMENTS

[« Older Comments](#)February 29, 2016 **belsin**

sorry I need more detail about this please help me brother send pdf or video to belsinben@gmail.com

November 2, 2016 [Sujata Made](#)

what is need of ic cd4049 in this circuit?

November 4, 2016 [Sujata Made](#)

Please send me EAGLE design(pcb design) and tell me more about power supply used....email id:mesujatamade@gmail.com

December 8, 2016 [craig](#)

This circuit is awesome. I was planning on building a simple voltmeter but now I going to give this more complex version a try. Thanks!

[« Older Comments](#)

Add a Comment

Your email address will not be published. Required fields are marked *

About us

- [About us](#)
- [Contact us](#)
- [Get new post via email](#)
- [Privacy policy](#)
- [Sitemap](#)

Projects for you

- [0-50V 3A DC Variable](#)
- [100W inveter](#)
- [1200W MOSFET Amplifier](#)
- [5V,6V,9V,12V DC Regulator](#)
- [LED Chaser circuit](#)
- [TDA2050 Amps](#)

Most Post

- [20W Integrated Amplifier](#)
- [Automatic battery charger](#)
- [Digital clock circuit with alarm](#)
- [My first Variable DC Power Supp](#)

